



*Bharati*

*Practical*  
**PHYSICS**

**Note Book**



MJC-4 Physics.

# Certificate

Name : ..... Class : .....

Roll No. : ..... Exam. No. : .....

Institution : .....

This is certified to be bonafide work of the student in the  
..... Laboratory during the academic  
year 20 .

No. of practicals certified ..... out of ..... in the subject of  
.....  
.....

Teacher in-charge

.....  
Examiner's Signature

.....  
Principal Signature

Date : .....

Institution Rubber Stamp

(N.B. : The candidate is expected to retain his/her journal till he/she passes in the subject.)


Practical - 2

\* Aim :-  
Describe the theory of determination of Self Inductance of a coil by Anderson Bridge.

\* Apparatus :-  
Apparatus required are, resistance boxes, capacitor, headphone, signal generator, inductance coil and connection wire.

\* Theory :-  
AC bridges are often used to measure the value of unknown impedance (Self/mutual inductance of inductors ~~or~~ or the capacitance of capacitors accurately).

Teacher's Signature : .....

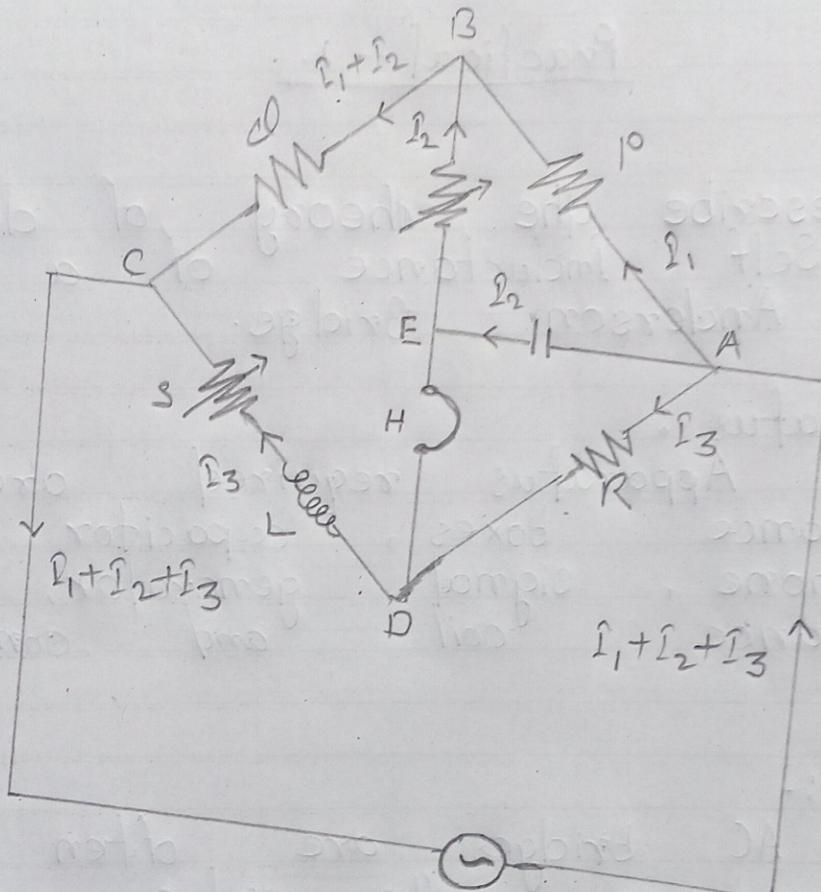

A large number of AC bridges are available and Anderson's Bridge is an AC bridge used to measure self inductance of the coil.

It is a modification of Wheatstone's Bridge. It enables us to measure the inductance of a coil using capacitor and resistors and does not require repeated balancing of the bridge. The connections are shown in fig: 1

The bridge is balanced by a steady current by replacing the headphone H by moving coil galvanometer and A.C source by a battery. This is done by adjusting the variable resistance. After a steady balance has been obtained. inductive

balance is obtained by using the AC source and headphones.

The condition for balance is that potentials of the terminals D and E are same. Then the current flowing through branch AB is  $I_1$ , through AE and EB is  $I_2$ . The current flowing through branches AD and DC is  $I_3$ , while that through branch BE is  $I_1 + I_2$ . No current flows through branch DE.

\* Circuit Details :-

Consider the mesh ABCDA

$$I_1 P + (I_1 + I_2) Q - I_3 (jL\omega + S) - I_3 R = 0$$

$$I_1 (P + Q) + I_2 Q = I_3 (S + R + jL\omega) \quad \text{--- (1)}$$

The shows that potential drop along ABC is equal to that along ADC

Consider the mesh ABEA, there is no e.m.f

$$I_1 P - I_2 r - \frac{I_2}{j\omega C} = 0$$

$$I_1 P - I_2 \left( r + \frac{1}{j\omega C} \right) = 0 \quad \text{--- (2)}$$

Consider the mesh AEDA,

$$\frac{I_2}{j\omega C} = I_3 R \quad \text{--- (3)}$$

i.e. potential difference from A to E is equal to that from A to D  
from (3) we get,

$$I_2 = j I_3 C \omega R \quad \text{--- (4)}$$

Now substitute the value of  $I_3$  from (1) in (4)

$$I_2 \left[ \frac{s + R + j\omega C R}{j\omega C R} - 0 \right] = I_1 [P + 0] \quad \text{--- (5)}$$

Dividing (5) by (2)

$$\frac{I_1(P+Q)}{I_1 P} = \frac{I_2 \left[ \frac{s+R+jL\omega}{jC\omega R} - Q \right]}{I_2 \left[ r + \frac{1}{jC\omega} \right]}$$

$$\Rightarrow \frac{P+Q}{P} \left[ r + \frac{1}{jC\omega} \right] = \frac{R+S+jL\omega - jC\omega RQ}{jC\omega R} \quad \text{--- (6)}$$

Multiply and divide by R in the L.H.S of (6) and rearrange,

$$\frac{(P+Q)R}{P} \left[ \frac{rjC\omega + 1}{jC\omega R} \right] = \frac{R+S+jL\omega - jC\omega RQ}{jC\omega R}$$

$$\Rightarrow PR + RQ + jPrc\omega R + j\omega rC\omega R = PR + PS + jL\omega P - PRjC\omega Q$$

$$\Rightarrow RQ + j(P+Q)RC\omega r = PS + j[L\omega - RC\omega Q]P \quad \text{--- (7)}$$

Equating real parts on both sides of (7)

$$\boxed{\frac{R}{S} = \frac{P}{Q}} \quad \text{--- (8)}$$

Teacher's Signature : .....

~~Equating real parts~~

Equating (8) represents the condition for balancing of the bridge.  
Equating imaginary parts on both sides of (7)

$$L = \frac{RC [Pr + dr + Pd]}{P} \quad \text{--- (9)}$$

Substituting:

$$S = \frac{Rd}{P}$$

From (8) and (9) gives us.

$$L = C [Rd + r(R+S)] \quad \text{--- (10)}$$

At this condition of ~~the~~ balancing there is minimum sound in the headphone.

further we can make  $P = d$

$$L = CR (P + 2r) \quad \text{--- (11)}$$

Teacher's Signature : .....

The inductive reactance can be calculated by

$$X_L = 2\pi fL$$

NO.	Resistance $R(\Omega)$	Resistance $Q(\Omega)$	Resistance $P(\Omega)$	Variable $S(\Omega)$	Variable Resistance $r(\Omega)$	Inductance $L(H)$
1.	200	200	200	200	50	0.0009
2.	200	200	200	200	55	0.0010
3.	200	200	200	200	60	0.0011
4.						

### Calculation

Given that

$$R = 200\Omega, Q = 200\Omega, S = 200\Omega, r = 50\Omega$$

$$C = 1 \times 10^{-8} F$$

Teacher's Signature : .....

$$L = C [RQ + r(R+S)]$$

$$\Rightarrow L = 1 \times 10^{-8} [(200 \times 200) + 30(200 + 200)]$$

$$\Rightarrow L = 1 \times 10^{-8} [40000 + 20000]$$

$$\Rightarrow L = 1 \times 10^{-8} \times 60000$$

$$\Rightarrow L = 6 \times 10^{-4} \text{ H} = 0.0006 \text{ H}$$

$$L = 0.0006 \text{ H}$$

$$X_L = 2\pi fL$$

$$\Rightarrow X_L = 2 \times 3.14 \times 1000 \times 0.001$$

$$\Rightarrow X_L = 6.28 \Omega$$

Result

$$L \approx 1 \times 10^{-5} \text{ H}$$

$$\text{and } X_L \approx 6.28 \Omega$$

Teacher's Signature : .....

Expt - 2,\* Aim :-

To determine the figure of merit of a table galvanometer, voltage sensitivity of the galvanometer, current required for half scale deflection (15 divisions) and full scale deflection (30 divisions) of galvanometer


\* Apparatus required :

Battery (2V), three resistance boxes, key, commutator, table galvanometer, connecting wires, etc.

\* Circuit :-

A battery of emf 2V is connected in series with two resistance boxes P and Q through a key K. A resistance box R is connected in parallel from the

Teacher's Signature : .....

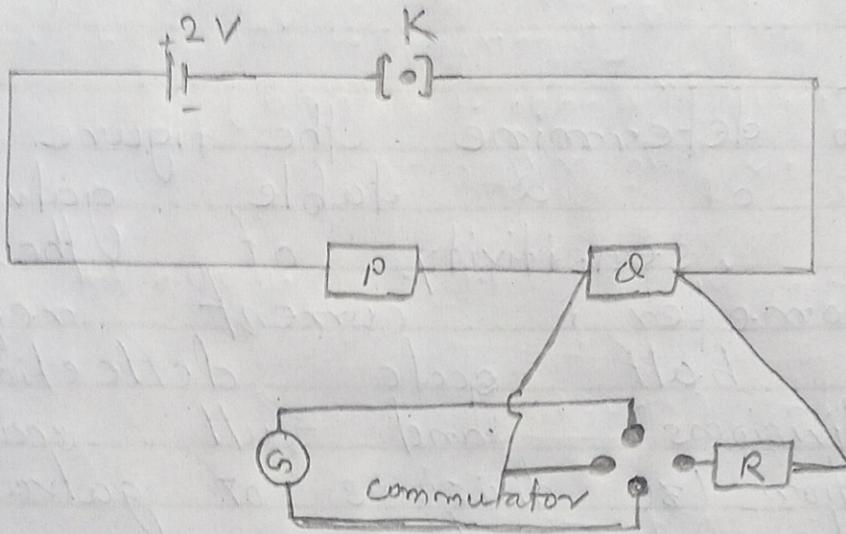

Figure

two terminals of  $\mathcal{D}$  through the commutator. A stable galvanometer is connected from the other two terminals of the commutator.

\* formula:-

(i) figure of merit of galvanometer

$$= \frac{E}{(P+d)} \cdot \frac{1}{G} \cdot \frac{d}{\mathcal{D}} \text{ amperes/div}$$

Where,  $E$  = emf of the battery

$P$  and  $d$  = resistance in  $\mathcal{R}$  box

$G$  = galvanometer

$\mathcal{D}$  = deflection observed.

(ii) Current required for half scale deflection =  $15 \times$  figure of merit (ampere)

(iii) Current required for full scale deflection =  $30 \times$  figure of merit (ampere)

Teacher's Signature : .....

① Voltage sensitivity of the galvanometer  
 $= G \times \text{Figure of merit (Volt/div)}$

S.No.	P ( $\Omega$ )	d ( $\Omega$ )	Deflections (div)			R for half deflection			R = G ( $\Omega$ )	d/d ( $\Omega$ /div)
			$\theta_1$	$\theta_2$	Mean $\theta$	$R_1 \Omega$	$R_2 \Omega$	Mean R( $\Omega$ )		
1	982	18	27	28	27.5	85	80	82.5	82.5	0.65
2	985	15	23	23	23	80	82	81.0	91.0	0.65
3	988	12	20	19	19.5	80	87	83.5	83.5	0.62
4	991	09	16	15	15.5	83	82	82.5	82.5	0.58
5	994	06	11	10	10.5	83	85	84.0	84.0	0.57

$$\text{Mean} = \frac{0.65 + 0.65 + 0.62 + 0.58 + 0.57}{5}$$

$$\text{Mean (d/d)} = 0.61 \Omega/\text{div}$$

$$G = 8.27 \Omega \approx 83 \Omega$$

$$\textcircled{1} K = 14.7 \mu\text{A}/\text{div} \quad \textcircled{2} I_{\text{half}} = 2.2 \times 10^{-4} \text{A}$$

$$\textcircled{3} I_{\text{full}} = 4.4 \times 10^{-4} \text{A}$$

$$G \times K = 1.22 \times 10^{-3} \text{V}/\text{div}$$

Ans

Teacher's Signature : .....